

NCERT Physics 12.7 Q6

EE23BTECH11212 - SWATHI DEEPIKA*

Question: Obtain the resonant frequency of a series LCR circuit with $L = 2.0\text{ H}$, $C = 32\text{ }\mu\text{F}$, and $R = 10\text{ }\Omega$. What is the Q-value of the circuit.

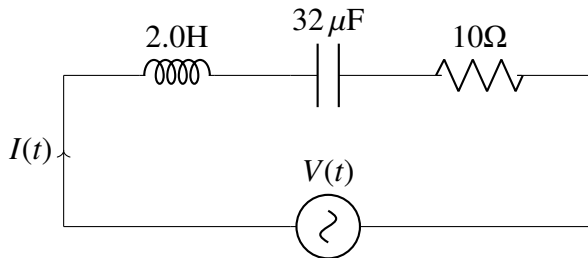


Fig. 1. LCR Circuit

Solution: In Figure Fig. 1 the following information is provided:

Symbol	Value	Description
L	2.0 H	Inductance
C	$32\text{ }\mu\text{F}$	Capacitance
R	$10\text{ }\Omega$	Resistance
Q	$\frac{\omega_r}{\Delta\omega}$	Quality Factor

TABLE I
PARAMETERS

SERIES LCR CIRCUIT ANALYSIS

Now, the voltage transfer function ($\frac{V(s)}{I(s)} = H(s)$) is given by Ohm's Law in the Laplace domain:

$$\frac{V(s)}{I(s)} = R + sL + \frac{1}{sC} \quad (1)$$

Now, after substitution the equation is

$$\frac{V(s)}{I(s)} = 10 + 2s + \frac{1}{32 \times 10^{-6}s} \quad (2)$$

This is the voltage transfer function for the series LCR circuit in the Laplace domain.

Resonant Frequency (ω_0):

At resonance, the impedance is purely resistive, meaning the imaginary part of $Z(s)$ is zero.

$$\text{Im}\{Z(s)\} = \omega L - \frac{1}{\omega C} = 0 \quad (3)$$

Solving for ω_0 :

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (4)$$

Substituting values:

$$\omega_0 = \frac{1}{\sqrt{2\text{ H} \times 32\text{ }\mu\text{F}}} = 125\text{ rad/s} \quad (5)$$

Quality Factor (Q) Calculation:

$$\frac{\omega_r}{\Delta\omega} = \frac{\omega_0 L}{R} \quad (6)$$

$$Q = \frac{\omega_0 L}{R} = \frac{125\text{ rad/s} \times 2\text{ H}}{10\text{ }\Omega} = 25 \quad (7)$$

Therefore, the quality factor of the LCR circuit is 25.

The equivalent s domain of the circuit is :

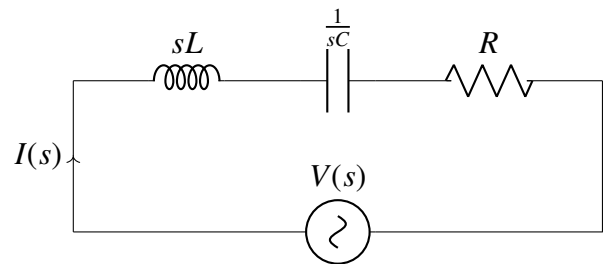


Fig. 2. LCR Circuit in s-domain