

Analog Assignment-1

Name -: Varasala Swathi Deepika

Roll no -: EE23BTECH11061

Problem Assigned -: 12.7.6

Abstract—Obtain the resonant frequency of a series of LCR circuit with $L=2.0\text{H}$, $C=32\mu\text{F}$ and $R=10\text{ ohm}$. What is the Q -value of this circuit?

Substituting the values:

$$Q = \frac{1}{10\ \Omega} \sqrt{\frac{2.0\text{ H}}{32 \times 10^{-6}\text{ F}}}$$

Calculating Q :

$$Q \approx \frac{1}{10} \times \sqrt{\frac{2.0}{0.000064}} \approx \frac{1}{10} \times \sqrt{31250} \approx \frac{1}{10} \times 177.05 \approx 17.71$$

Therefore, the resonant frequency is $f_0 \approx 19.90\text{ Hz}$ and the quality factor is $Q \approx 17.71$.


SOLUTION -:

In Exercise 7.18, the following information is provided:

Component	Value	Unit
Inductor	2.0	H
Capacitor	32μ	F
Resistance	10	ohm

TABLE 0

ELECTRICAL COMPONENT PARAMETERS

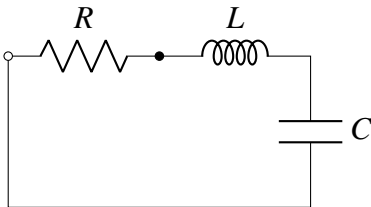

Given values: $L = 2.0\text{ H}$, $C = 32 \times 10^{-6}\text{ F}$, $R = 10\ \Omega$.

The resonant frequency f_0 is given by:

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

Substituting the values:

$$f_0 = \frac{1}{2\pi \sqrt{(2.0\text{ H})(32 \times 10^{-6}\text{ F})}}$$

Calculating f_0 :

$$f_0 \approx \frac{1}{2\pi \sqrt{0.000064}} \approx \frac{1}{2\pi \times 0.008} \approx \frac{1}{0.05027} \approx 19.90\text{ Hz}$$

The quality factor Q is given by:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$