

1. **analog question**

Question: Obtain the resonance frequency of a series LCR circuit with $L = 2.0\text{ H}$, $C = 32\text{ }\mu\text{F}$, and $R = 10\text{ }\Omega$. What is the Q-value of the circuit.