

# NCERT Physics 12.7 Q6

EE23BTECH11061 - SWATHI DEEPIKA\*

**Question:** Obtain the resonance frequency of a series LCR circuit with  $L = 2.0\text{ H}$ ,  $C = 32\text{ }\mu\text{F}$ , and  $R = 10\text{ }\Omega$ . What is the Q-value of the circuit.

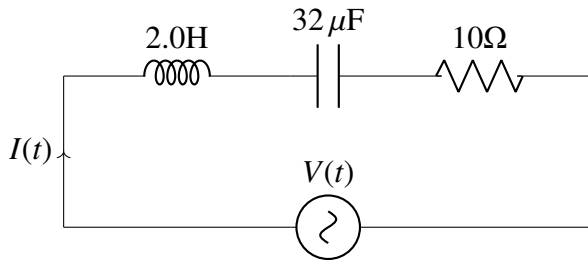


Fig. 1. LCR Circuit

**Solution:**

Symbol	Value	Description
$L$	$2.0\text{ H}$	Inductance
$C$	$32\text{ }\mu\text{F}$	Capacitance
$R$	$10\text{ }\Omega$	Resistance
$Q$	$\frac{V_L}{V_R}$	Quality Factor
$V_L$	$sLI(s)$	Voltage across inductance
$V_C$	$RI(s)$	Voltage across capacitor

TABLE I  
PARAMETERS

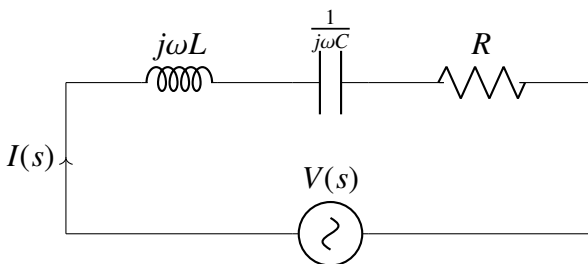


Fig. 2. LCR Circuit

From Fig. 2,

$$V(s) = RI(s) + sLI(s) + \frac{1}{sC}I(s) \quad (1)$$

$$= I(s) \left( R + Ls + \frac{1}{sC} \right) \quad (2)$$

$$\Rightarrow I(s) = \frac{V(s)}{\left( R + Ls + \frac{1}{sC} \right)} \quad (3)$$

At resonance,

$$Ls + \frac{1}{sC} = 0 \quad (4)$$

$$\Rightarrow s = j \frac{1}{\sqrt{LC}} \quad (5)$$

$s$  in terms of angular resonance frequency as

$$s = j\omega_0 \quad (6)$$

From (5) and (6), we get

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (7)$$

2) Quality Factor

a) voltage across inductor,

$$Q = \left( \frac{V_L}{V_R} \right)_{\omega_0} = \frac{|sLI(s)|}{|RI(s)|} \quad (8)$$

$$= \frac{1}{\sqrt{LC}} \frac{L}{R} \quad (9)$$

$$= \frac{1}{R} \sqrt{\frac{L}{C}} \quad (10)$$

b) Using voltage across capacitor,

$$Q = \left( \frac{V_C}{V_R} \right)_{\omega_0} = \frac{\left| \frac{I(s)}{sC} \right|}{|RI(s)|} \quad (11)$$

$$= \frac{\sqrt{LC}}{RC} \quad (12)$$

$$= \frac{1}{R} \sqrt{\frac{L}{C}} \quad (13)$$

3) Plot of Impedance vs Angular Frequency

$$H(s) = \frac{V(s)}{I(s)} \quad (14)$$

1) Frequency Response of the Circuit

Using (3),

$$H(s) = R + sL + \frac{1}{sC} \quad (15)$$

$$\Rightarrow H(j\omega) = R + j\omega L + \frac{1}{j\omega C} \quad (16)$$

$$\Rightarrow |H(j\omega)| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} \quad (17)$$

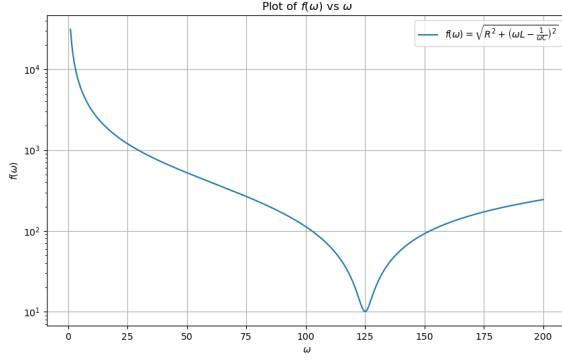


Fig. 3. Impedance vs  $\omega$  (using values in Table I)

Substituting values,

$$\omega_0 = \frac{1}{\sqrt{(2.0)(32 \times 10^{-6})}} \quad (18)$$

$$\omega_0 = \frac{1}{\sqrt{64 \times 10^{-6}}} \quad (19)$$

$$\omega_0 = \frac{1}{8 \times 10^{-3}} \quad (20)$$

$$\omega_0 = 125 \text{ Hz} \quad (21)$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (22)$$

$$Q = \frac{1}{10} \sqrt{\frac{2}{32 \times 10^{-6}}} \quad (23)$$

$$Q = \frac{100}{4} \quad (24)$$

$$Q = 25 \quad (25)$$