

1. **12.7 6th analog question**

**Question:** Obtain the resonance frequency of a series LCR circuit with  $L = 2.0\text{ H}$ ,  $C = 32\text{ }\mu\text{F}$ , and  $R = 10\text{ }\Omega$ . What is the Q-value of the circuit.