

NCERT Physics 12.7 Q6

EE23BTECH11061 - SWATHI DEEPIKA*

Question: Obtain the resonance frequency of a series LCR circuit with $L = 2.0\text{ H}$, $C = 32\text{ }\mu\text{F}$, and $R = 10\text{ }\Omega$. What is the Q-value of the circuit.

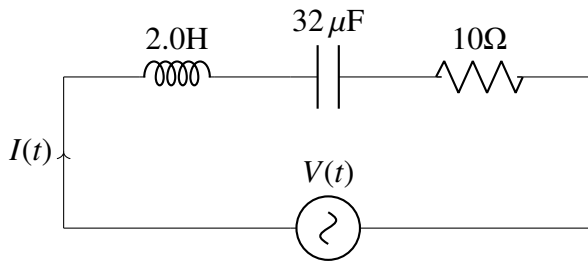


Fig. 1. LCR Circuit

Solution: In Figure Fig. 1 the following information is provided:

| Symbol | Value | Description |
|--------|-------------------------|---------------------------|
| L | 2.0 H | Inductance |
| C | $32\text{ }\mu\text{F}$ | Capacitance |
| R | $10\text{ }\Omega$ | Resistance |
| Q | $\frac{V_L}{V_R}$ | Quality Factor |
| V_L | $sLI(s)$ | Voltage across inductance |
| V_C | $RI(s)$ | Voltage across capacitor |

TABLE I
PARAMETERS

The equivalent s domain of the circuit is :

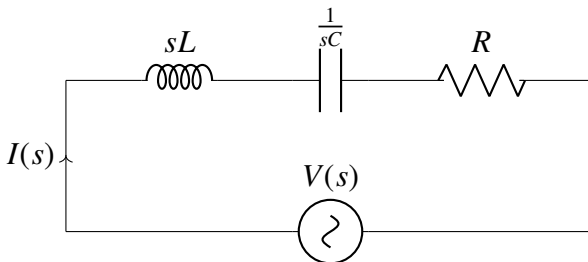


Fig. 2. LCR Circuit in s-domain

Now, the voltage transfer function ($\frac{V(s)}{I(s)} = H(s)$) is given by Ohm's Law in the Laplace domain:

$$\frac{V(s)}{I(s)} = R + sL + \frac{1}{sC} \quad (1)$$

At resonance, the circuit becomes purely resistive. The reactances of capacitor and inductor cancel out as follows:

$$sL + \frac{1}{sC} = 0 \quad (2)$$

$$\Rightarrow s = j\frac{1}{\sqrt{LC}} \quad (3)$$

s can be expressed in terms of resonant frequency as

$$s = j\omega_0 \quad (4)$$

Comparing equations (3) and (4), we get

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (5)$$

Quality Factor (Q) of an LCR circuit is defined as the ratio of voltage across inductor or capacitor to that across the resistor at resonance.

The voltage across inductor is :

Assuming a sinusoidal current $I_s(t) = I_0 \sin(\omega t + \phi)$, where:

Now, differentiate $I_s(t)$ with respect to time to find $\frac{di}{dt}$.

$$\frac{di}{dt} = I_0 \omega \cos(\omega t + \phi). \quad (6)$$

Now, substitute $\frac{di}{dt}$ into the equation for voltage across the inductor:

$$V_s = L \frac{di}{dt} \quad (7)$$

$$= LI_0 \omega \cos(\omega t + \phi). \quad (8)$$

Express the cosine term using Euler's formula:

$$\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}. \quad (9)$$

Substitute this into the equation:

$$V_s = LI_0\omega \left(\frac{e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)}}{2} \right). \quad (10)$$

Simplify further:

$$V_s = j\omega LI_0 \sin(\omega t + \phi). \quad (11)$$

$$V_s = j\omega LI_s. \quad (12)$$

$$V_s = sLI_s. \quad (13)$$

The voltage across resistor is :

By Ohm's Law, we know that $V = IR$. So, the voltage across a resistor (V_R) is given by $I_s \cdot R$. In mathematical form:

$$V_R = I_s \cdot R \quad (14)$$

So, the quality factor from (13) and (14) is :

$$Q = \left(\frac{V_L}{V_R} \right)_{\omega_0} = \frac{|sLI(s)|}{|RI(s)|} \quad (15)$$

$$\Rightarrow Q = \frac{1}{\sqrt{LC}} \frac{L}{R} \quad (16)$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (17)$$

The voltage transfer function after substituting the values in the (1) :

$$\frac{V(s)}{I(s)} = 10 + 2s + \frac{1}{32 \times 10^{-6}s} \quad (18)$$

$$H(s) = 10 + 2s + \frac{1}{32 \times 10^{-6}s} \quad (19)$$

The resonant frequency of the circuit from (5) :

$$\omega_0 = \frac{1}{\sqrt{2 \text{ H} \times 32 \mu\text{F}}} = 125 \text{ rad/s} \quad (20)$$

The resonant frequency is 125 rad/s.

The Quality factor of the circuit from (17) :

$$Q = \frac{1}{10} \sqrt{\frac{2}{32 \times 10^{-6}}} = \frac{1}{40 \times 10^{-3}} = 25 \quad (21)$$

Therefore, the quality factor of the LCR circuit is 25.

Plot the amplitude of the transfer function w.r.t omega :

$$H(s) = R + sL + \frac{1}{sC} \quad (22)$$

$$\Rightarrow H(j\omega) = R + j\omega L + \frac{1}{j\omega C} \quad (23)$$

$$\Rightarrow |H(j\omega)| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \quad (24)$$

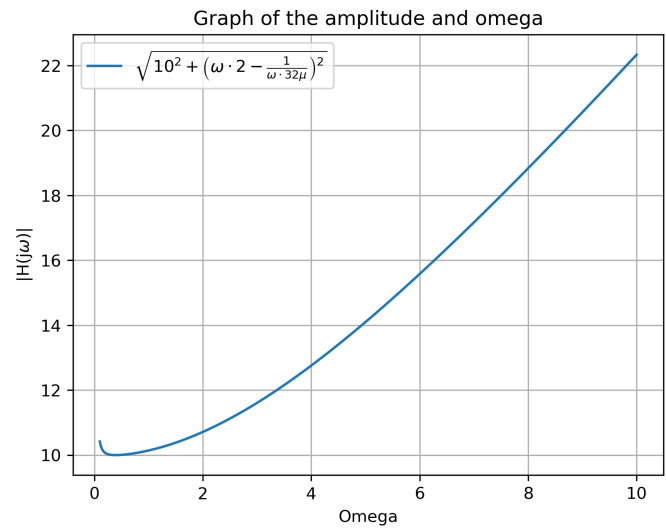


Fig. 3. Impedance vs ω