

NCERT Physics 12.7 Q6

EE23BTECH11061 - SWATHI DEEPIKA*

Question: Obtain the resonance frequency of a series LCR circuit with $L = 2.0\text{ H}$, $C = 32\text{ }\mu\text{F}$, and $R = 10\text{ }\Omega$. What is the Q-value of the circuit.

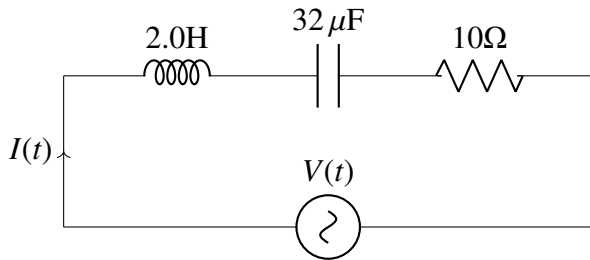


Fig. 1. LCR Circuit

Solution: In Figure Fig. 1 the following information is provided:

Symbol	Value	Description
L	2.0 H	Inductance
C	$32\text{ }\mu\text{F}$	Capacitance
R	$10\text{ }\Omega$	Resistance
Q	$\frac{V_L}{V_R}$	Quality Factor
V_L	$sLI(s)$	Voltage across inductance
V_C	$RI(s)$	Voltage across capacitor

TABLE I
PARAMETERS

The equivalent s domain of the circuit is :

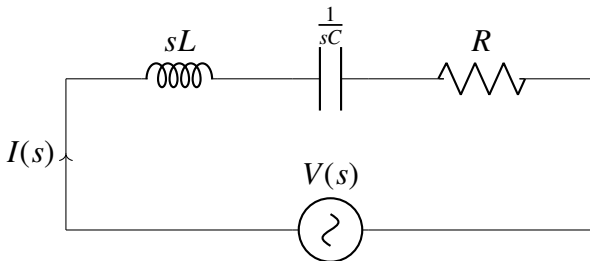


Fig. 2. LCR Circuit in s-domain

$$\frac{V(s)}{I(s)} = H(s) \quad (1)$$

$$\frac{V(s)}{I(s)} = R + sL + \frac{1}{sC} \quad (2)$$

At resonance,

$$Ls + \frac{1}{sC} = 0 \quad (3)$$

$$\Rightarrow s = j\frac{1}{\sqrt{LC}} \quad (4)$$

$$s = j\omega_0 \quad (5)$$

Comparing equations (4) and (5), we get

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (6)$$

$$I_s(t) = I_0 \sin(\omega t + \phi) \quad (7)$$

$$\frac{di}{dt} = I_0 \omega \cos(\omega t + \phi). \quad (8)$$

$$V_s = L \frac{di}{dt} \quad (9)$$

$$= LI_0 \omega \cos(\omega t + \phi). \quad (10)$$

$$\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}. \quad (11)$$

$$V_s = LI_0 \omega \left(\frac{e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)}}{2} \right). \quad (12)$$

$$V_s = j\omega LI_0 \sin(\omega t + \phi). \quad (13)$$

$$V_s = j\omega LI_s. \quad (14)$$

$$V_s = sLI_s. \quad (15)$$

$$V_R = I_s \cdot R \quad (16)$$

From (15) and (16) ,

$$Q = \left(\frac{V_L}{V_R} \right)_{\omega_0} = \frac{|sLI(s)|}{|RI(s)|} \quad (17)$$

$$\Rightarrow Q = \frac{1}{\sqrt{LC}} \frac{L}{R} \quad (18)$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} \quad (19)$$

$$\frac{V(s)}{I(s)} = 10 + 2s + \frac{1}{32 \times 10^{-6}s} \quad (20)$$

$$H(s) = 10 + 2s + \frac{1}{32 \times 10^{-6}s} \quad (21)$$

From, (6) :

$$\omega_0 = \frac{1}{\sqrt{2 \text{ H} \times 32 \mu\text{F}}} = 125 \text{ rad/s} \quad (22)$$

The resonant frequency is 125 *rad/s*.

From, (19) :

$$Q = \frac{1}{10} \sqrt{\frac{2}{32 \times 10^{-6}}} = \frac{1}{40 \times 10^{-3}} = 25 \quad (23)$$

Therefore, the quality factor of the LCR circuit is 25.

$$H(s) = R + sL + \frac{1}{sC} \quad (24)$$

$$\Rightarrow H(j\omega) = R + j\omega L + \frac{1}{j\omega C} \quad (25)$$

$$\Rightarrow |H(j\omega)| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2} \quad (26)$$

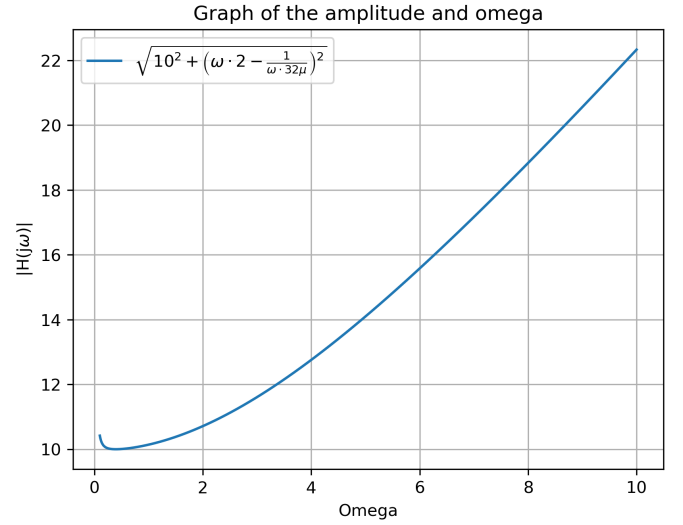


Fig. 3. Impedance vs ω